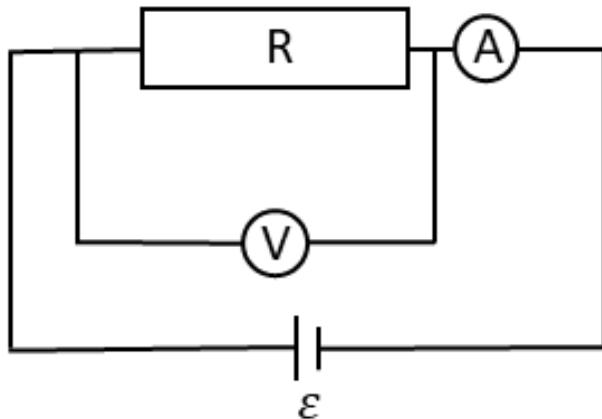


## Omov zakon za deo strujnog kola

Postupak izvođenja vežbe:

1) Povezati šemu:




- 2) Za različite vrednosti  $\epsilon$  očitati vrednosti struje i napona, pri čemu je  $R=\text{const}$ .
- 3) Nacrtati grafik zavisnosti napona od struje.
- 4) Grafičkim metodom odrediti otpornost  $R$ .

Rezultati merenja:

I [A]	U [V]	$\Delta I$ [A]	$\Delta U$ [V]
0.08	2.88	0.01	0.01
0.1	3.44	0.01	0.01
0.12	4.26	0.01	0.01
0.14	4.79	0.01	0.01
0.16	5.33	0.01	0.01
0.18	6.13	0.01	0.01
0.2	6.72	0.01	0.01
0.22	7.56	0.01	0.01
0.24	8.3	0.01	0.01
0.26	9.1	0.01	0.01
0.28	9.6	0.01	0.01

Xa	Ya	Xb	Yb
0.1	3.44	0.26	9.1
$\Delta X_a$	$\Delta Y_a$	$\Delta X_b$	$\Delta Y_b$
0.01	0.01	0.01	0.01
$a$		$\Delta a$	
35.375	4.54688		
$R$		$\Delta R$	
35.375	4.54688		

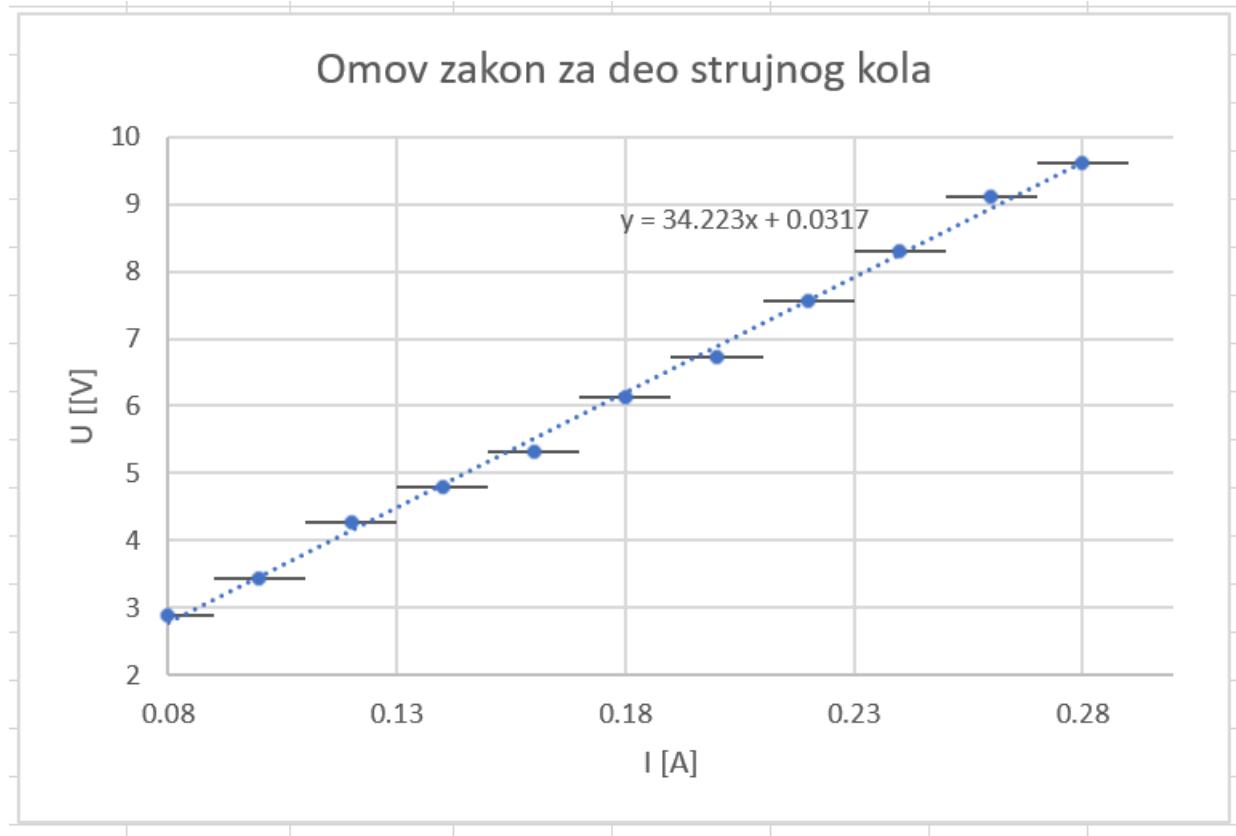

**Slika aparature:**

